

Assignment 1

Mission 1: Creating gates using NAND gates.


a) NOT gate Boolean Expression: $O = \overline{X \cdot X} = \overline{X}$



NOT gate

X	O
0	1
1	0

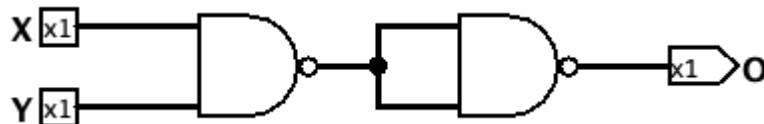
b) AND gate Boolean Expression: $O = \sim(\sim(X \cdot Y) \cdot \sim(X \cdot Y)) = X \cdot Y$



And gate

X	Y	O
0	0	0
0	1	0
1	0	0
1	1	1

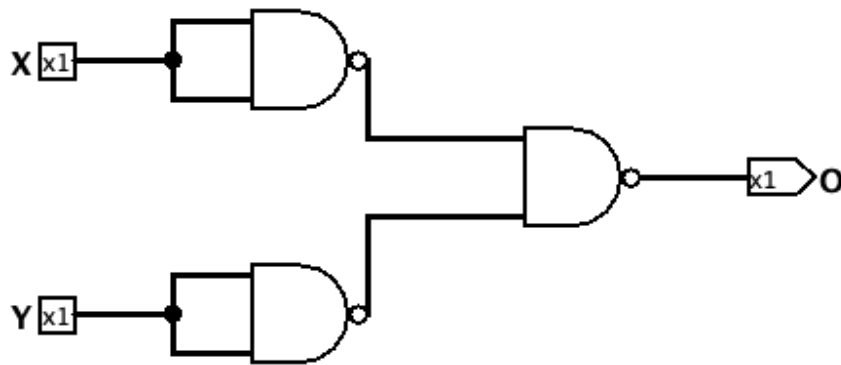c) OR gate Boolean Expression: $O = \sim(\sim(X \cdot X) \cdot \sim(Y \cdot Y)) = X + Y$



OR gate


X	Y	O
0	0	0
0	1	1
1	0	1
1	1	1

Mission 2 Making two-bit Half Adder:

a) Truth Table:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


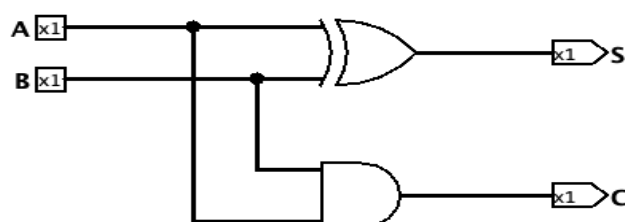
b) Boolean Expression: $S = A \oplus B$
 $C = A \cdot B$



c) Circuit:

Mission 3 Building a Smart Selector:

Boolean Expression: $O = I3 \cdot S0 \cdot S1 + I2 \cdot \sim S0 \cdot S1 + I1 \cdot S0 \cdot \sim S1 + I0 \cdot \sim S0 \cdot \sim S1$

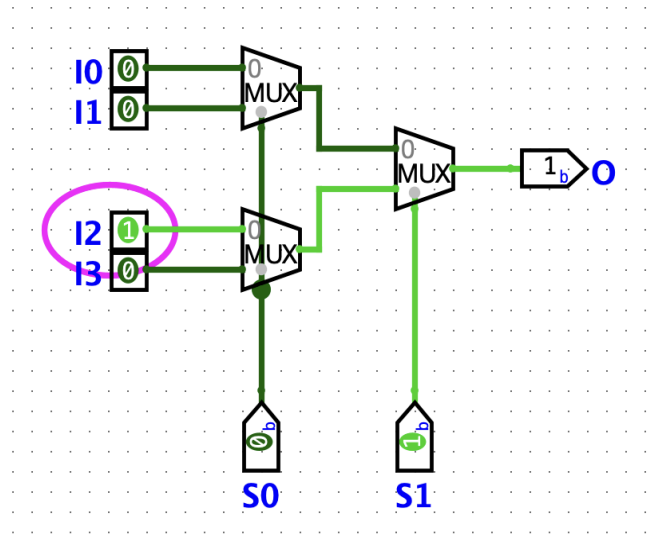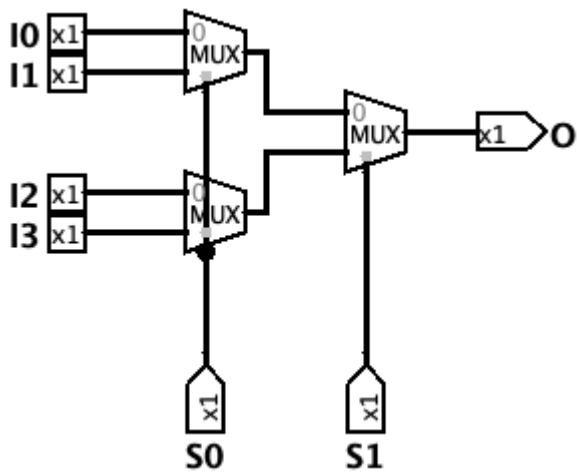

Mission 4: Pattern Detector

a) We will need 2 D flip-flops. Because in the state diagram(mealy/moore) of pattern recognition '111' , it will need 3 states (00,01,10). So to represent three different states, we will need 2 bits , thus 2 flip-flops.

Current State (Q_1Q_0)	Input (X)	Next State (D_1D_0)	Output (P)
S0 (00)	0	S0 (00)	0
S0 (00)	1	S1 (01)	0
S1 (01)	0	S0 (00)	0
S1 (01)	1	S2 (10)	0
S2 (10)	0	S0 (00)	0
S2 (10)	1	S2 (10)	1


b) If Q_1 is output of D_1 and Q_0 is output of D_0 , and P is our Output then:

$$D_1 = X \cdot (Q_1 \oplus Q_0)$$

$$D_2 = X \cdot (\overline{Q_1 + Q_0})$$

$$P = X \cdot Q_1 \cdot \overline{Q_0}$$

Therefore circuit will look be:

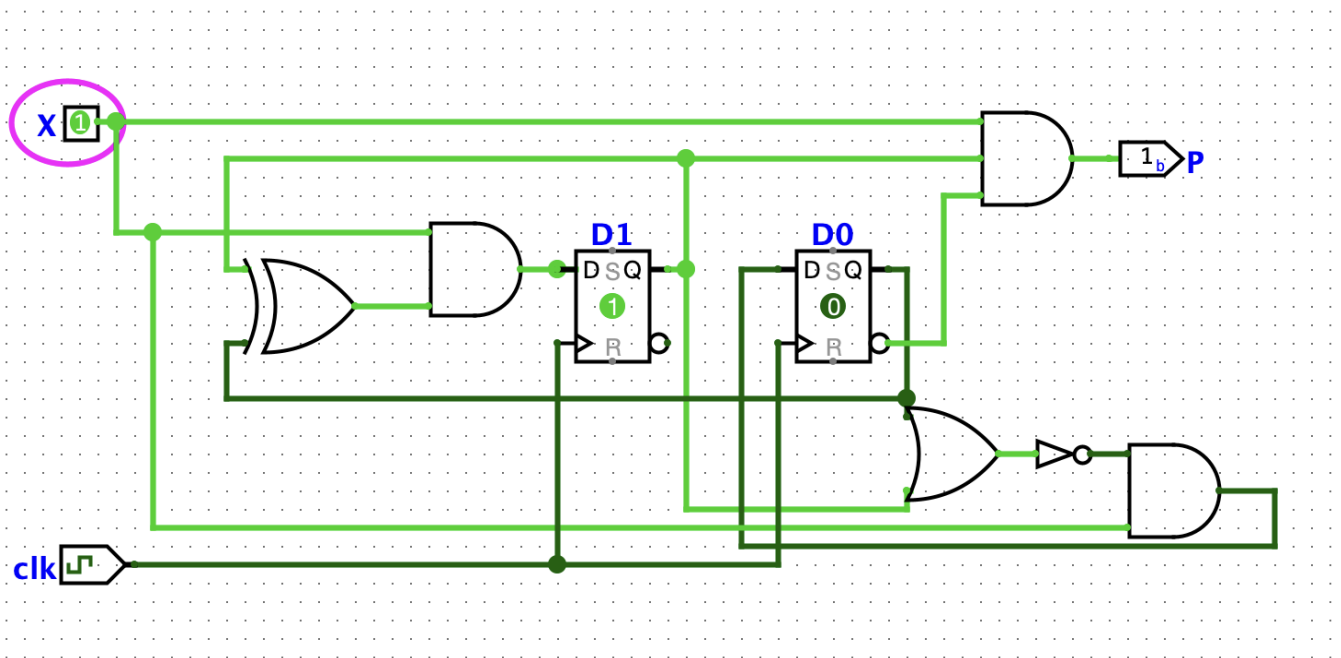

Mission 5: Designing 2-bit counter for sequence 00->01->10->11->00 using D flip-flops.

As it is a two bit counter ,it will use 2 D flip flops. Lets say our two flips-flops are D_1 and D_0 , and Q_1, Q_0 are their outputs respectively with Q_0 being the LSB.

a) State transition table will nothing but our desired sequence which will be:

Q_1	Q_0	D_1	D_0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

Here, Q_1 = Present state/ current output of D_1 flip flop.

Q_0 = Present state/ current output of D_0 flip flop.

D_1 = Next state / current input of D_1 flip flop.


D_0 = Next state / current input of D_0 flip flop.

b) Boolean expression derived from the above transition table would be:

$$D_1 = Q_1 \oplus Q_0$$

$$D_0 = \overline{Q_0}$$

c)

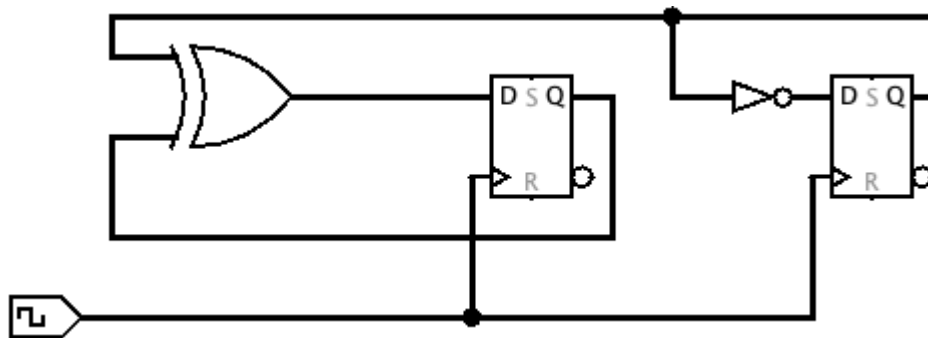

Link of video simulating counter: [📺 Counter_using_DFloplop.mov](#)

Name : Amanpreet Singh

Roll No: 251110009